

(Please write your Exam Roll No.)

Exam Roll No. 091402016

END TERM EXAMINATION

SECOND SEMESTER [BCA] MAY JUNE 2017

Paper Code: BCA-106

Subject: Digital Electronics
(Batch 2011 onwards)

Time: 3 Hours

Maximum Marks: 75

Note: Attempt any five questions including Q.no.1 which is compulsory.
Select one question from each unit.

- Q1 Attempt **any five** from the following:- (5x5=25)
- (a) Design full subtractor circuit using NAND gate only.
 - (b) Explain how transistor as a switch works? Give its use in logic circuits.
 - (c) Define fan-in, fan-out, propagation delay, noise margin and voltage parameters.
 - (d) Explain decoder and demultiplexer. Give their applications.
 - (e) State the De Morgan's theorem and prove them with an example.
 - (f) Define synchronous and asynchronous counters with their merit and demerits.

UNIT-I

- Q2 Simply the expressions:-
- (a) $AB + \overline{AC} + A\overline{B}C(AB + C)$ (3)
 - (b) Explain the operation and advantages of CMOS. (6.5)
 - (c) Prove $A + \overline{A}B = A + B$ (3)
- Q3
- (a) Design a combinational circuit whose input is three bit number and whose output is equal to square of input and implement it using basic gates. (6.5)
 - (b) Explain briefly the BCD to seven segment decoder. (6)

UNIT-II

- Q4
- (a) Design a full adder circuit using Multiplexer. (6.5)
 - (b) Implement the Ex-OR gate equation with NAND gates only. (6)
- Q5
- (a) Draw the logic diagram of parity checker and generator/checker. Explain its operation with the help of truth table. (6.5)
 - (b) Design a binary multiplier for following: A=1011, B=111 (6)

UNIT-III

- Q6
- (a) Define edge triggering in flip-flops. Explain Master slave JK flip-flop that solves the problem of Race-around condition, with diagram. (7)
 - (b) Design JK flip-flop using SR flip-flop. (5.5)
- Q7
- (a) Explain the bidirectional shift register with diagram, truth table and clock pulse. Give their applications. (7.5)
 - (b) Differentiate Static RAM and Dynamic RAM. (5)

UNIT-IV

- Q8
- (a) Design Modulo 7 counters with truth table and logic diagram. (7.5)
 - (b) Give the application of PLA and PLD. (5)
- Q9
- (a) Design a combinational circuit with PLA, having three inputs, four product terms and two outputs: (7.5)
 $F1(A,B,C)=\Sigma(3,5,6,7), F2(A,B,C)=\Sigma(0,2,4,7)$
 - (b) Explain Johnson's counter with truth table and clock pulses. (5)
